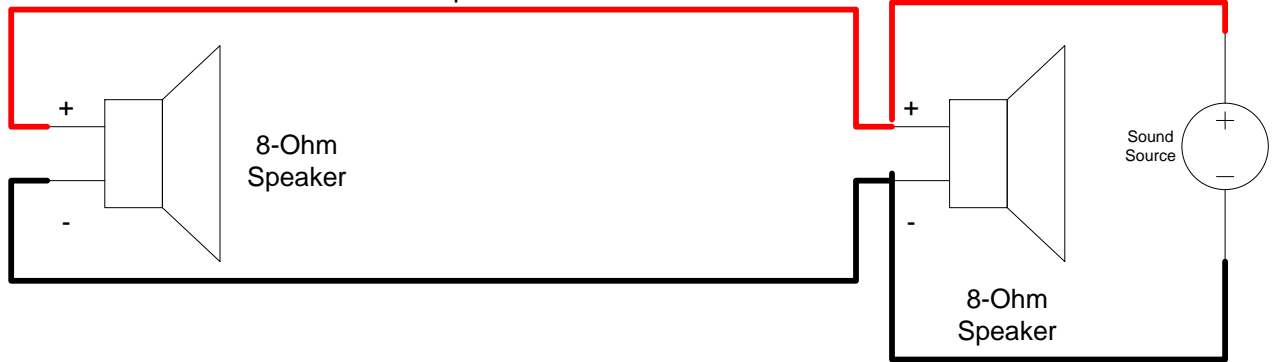
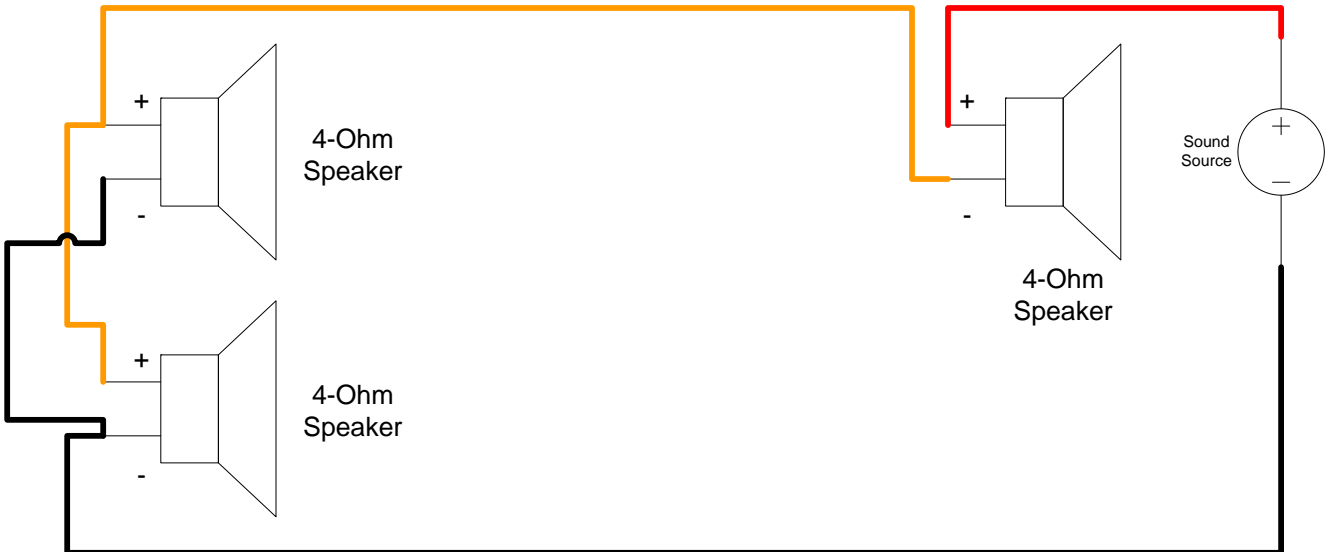


8-Ohm Speakers in Parallel (A-unit/A-Unit or A-unit/B-unit)
Net Impedance = 4 Ohms



4-Ohm Lead Unit wired in Series
With Parallel-connected 4-Ohm speakers in B-Unit
Net Impedance = 6 Ohms (takes advantage of extra
space in B-unit and allows A-unit to run solo)



4-Ohm Series-Parallel Connection for A-B-B-A
Speakers in All Units
Net Impedance = 4 Ohms
(allows lead A/B pair to run with slave A/B pair)

